



AMC

TEST

ME 4543: Mechatronics
Department of Mechanical Engineering
Mock Exam

Useful information:

- (1) There are 4 questions.
- (2) Each question has only 1 correct answer. Each question is worth 1 point and there is no negative marking.
- (3) Cellphones, laptops, tablets and other electronics except calculators should be shut down. Only calculators are allowed.
- (4) Darken the appropriate box next to the options entirely. Your answers will be graded by a computer so it is important that you darken the bubble entirely and do not write anything near the bubbles or options.


NOTE: The actual exam will have 20 questions worth 20 points.

Firstname and Lastname:

Part 1

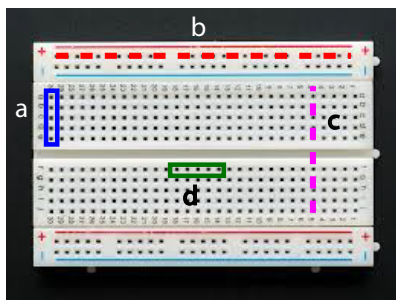Question 1 Consider the breadboard below. Indicate the true statement

- Holes shown by the blue vertical box denoted by a are all connected
- Three options are true
- Holes shown by the pink vertical line denoted by c are all connected
- Holes shown by the red dashed line denoted by b are all connected
- Two options are true




Question 2 For the waveform $y(t) = 10 \sin(\pi) + 5 \cos(\pi)$, the DC offset is

- 15
- 12
- 5
- 0
- 11

Question 3 A voltage source $V = 10 \text{ V}$, resistors R_1 and $R_2 = 20 \Omega$ are in all series. If the voltage drop across the R_1 resistor is 2.5 V then R_1 in Ω is

- 10
- 5
- 7.5
- 3.33
- 6.67

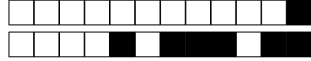

Question 4 A voltage source V_s is connected in series with two resistors $R_1 = 1 \Omega$ and $R_2 = 2 \Omega$. If voltage drop across R_1 is 1 V then V_s in V is

- 1.2
- 8
- 12
- 3
- 0

Question 5 Consider two resistances, $R_1 = 5 \Omega$ and $R_2 = 10 \Omega$. The two resistors when connected in series, have an effective resistance R_{series} and when connected in parallel, have an effective resistance $R_{parallel}$. Indicate all true statements.

- $R_{series} > R_1$
- $R_2 > R_{parallel}$
- $R_{parallel} > R_{series}$
- Two options are true
- Three options are true

Question 6 A resistor has a value of 50 M Ω . The second band is black. The third band will be

- Red
- Blue
- Orange
- Violet


Question 7 Two capacitors of values $2\mu F$ each as connected in series. The equivalent capacitance in μF is

- 1
- 0.5
- 2
- 4
- 8



Question 8 In the circuit shown if $V_a = 10\text{ V}$ and $V_b = 5\text{ V}$ then V_{out} in V equals

- Three options are true
- Two options are true
- $R_2 > R_{parallel}$
- $R_{series} > R_1$
- $R_{parallel} > R_{series}$

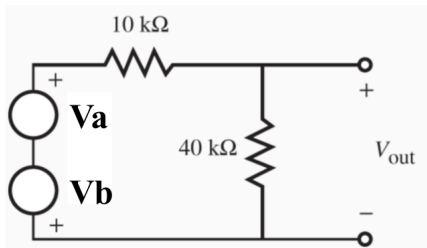



ME 4543: Mechatronics
Department of Mechanical Engineering
Mock Exam

Useful information:

- (1) There are 4 questions.
- (2) Each question has only 1 correct answer. Each question is worth 1 point and there is no negative marking.
- (3) Cellphones, laptops, tablets and other electronics except calculators should be shut down. Only calculators are allowed.
- (4) Darken the appropriate box next to the options entirely. Your answers will be graded by a computer so it is important that you darken the bubble entirely and do not write anything near the bubbles or options.


NOTE: The actual exam will have 20 questions worth 20 points.

Firstname and Lastname:

Part 1

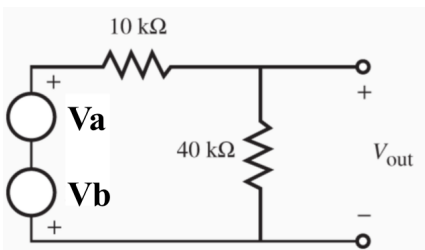
Question 1 In the circuit shown if $V_a = 10\text{ V}$ and $V_b = 5\text{ V}$ then V_{out} in V equals

- $R_{parallel} > R_{series}$
- Three options are true
- $R_{series} > R_1$
- $R_2 > R_{parallel}$
- Two options are true



Question 2 Two capacitors of values $2\mu F$ each as connected in series. The equivalent capacitance in μF is

- 1
- 8
- 2
- 4
- 0.5

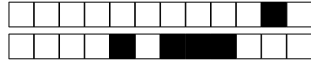


Question 3 Consider two resistances, $R_1 = 5 \Omega$ and $R_2 = 10 \Omega$. The two resistors when connected in series, have an effective resistance R_{series} and when connected in parallel, have an effective resistance $R_{parallel}$. Indicate all true statements.

- Three options are true
- $R_{parallel} > R_{series}$
- $R_2 > R_{parallel}$
- $R_{series} > R_1$
- Two options are true

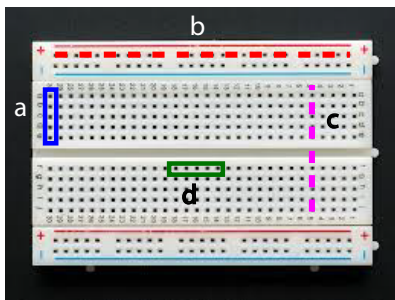Question 4 Consider the breadboard below. Indicate the true statement

- Holes shown by the pink vertical line denoted by c are all connected
- Two options are true
- Three options are true
- Holes shown by the red dashed line denoted by b are all connected
- Holes shown by the blue vertical box denoted by a are all connected



Question 5 A voltage source V_s is connected in series with two resistors $R_1 = 1 \Omega$ and $R_2 = 2 \Omega$. If voltage drop across R_1 is 1 V then V_s in V is

- 0
- 12
- 1.2
- 8
- 3

Question 6 For the waveform $y(t) = 10 \sin(\pi t) + 5 \cos(\pi t)$, the DC offset is

- 15
- 0
- 12
- 11
- 5

Question 7 A voltage source $V = 10 \text{ V}$, resistors R_1 and $R_2 = 20 \Omega$ are in all series. If the voltage drop across the R_1 resistor is 2.5 V then R_1 in Ω is

- 5
- 3.33
- 7.5
- 6.67
- 10



+2/3/55+

Question 8 A resistor has a value of $50 \text{ M } \Omega$. The second band is black. The third band will be

- Orange
- Violet
- Red
- Blue



AMC

TEST

ME 4543: Mechatronics
Department of Mechanical Engineering
Mock Exam

Useful information:

- (1) There are 4 questions.
- (2) Each question has only 1 correct answer. Each question is worth 1 point and there is no negative marking.
- (3) Cellphones, laptops, tablets and other electronics except calculators should be shut down. Only calculators are allowed.
- (4) Darken the appropriate box next to the options entirely. Your answers will be graded by a computer so it is important that you darken the bubble entirely and do not write anything near the bubbles or options.

NOTE: The actual exam will have 20 questions worth 20 points.

Firstname and Lastname:
.....


Part 1

Question 1 A voltage source V_s is connected in series with two resistors $R_1 = 1 \Omega$ and $R_2 = 2 \Omega$. If voltage drop across R_1 is 1 V then V_s in V is

- 1.2
- 3
- 12
- 8
- 0

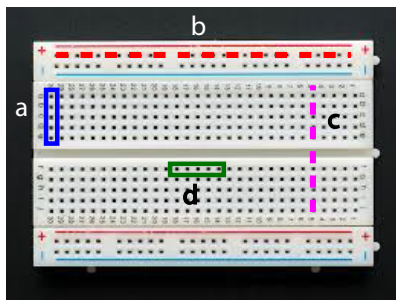Question 2 Consider the breadboard below. Indicate the true statement

- Two options are true
- Holes shown by the pink vertical line denoted by c are all connected
- Three options are true
- Holes shown by the blue vertical box denoted by a are all connected
- Holes shown by the red dashed line denoted by b are all connected



Question 3 A voltage source $V = 10 \text{ V}$, resistors R_1 and $R_2 = 20 \Omega$ are in all series. If the voltage drop across the R_1 resistor is 2.5 V then R_1 in Ω is

- 3.33
- 10
- 7.5
- 6.67
- 5




Question 4 Two capacitors of values $2\mu F$ each as connected in series. The equivalent capacitance in μF is

- 8
- 0.5
- 2
- 4
- 1

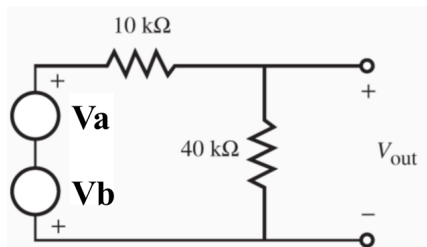Question 5 In the circuit shown if $V_a = 10\text{ V}$ and $V_b = 5\text{ V}$ then V_{out} in V equals

- Two options are true
- $R_{parallel} > R_{series}$
- $R_2 > R_{parallel}$
- $R_{series} > R_1$
- Three options are true



Question 6 A resistor has a value of $50\text{ M}\Omega$. The second band is black. The third band will be

- Orange
- Blue
- Red
- Voilet

Question 7 For the waveform $y(t) = 10\sin(\pi t) + 5\cos(\pi t)$, the DC offset is

- 11
- 5
- 0
- 12
- 15

Question 8 Consider two resistances, $R_1 = 5\ \Omega$ and $R_2 = 10\ \Omega$. The two resistors when connected in series, have an effective resistance R_{series} and when connected in parallel, have an effective resistance $R_{parallel}$. Indicate all true statements.

- $R_{parallel} > R_{series}$
- $R_{series} > R_1$
- $R_2 > R_{parallel}$
- Two options are true
- Three options are true



+3/3/52+



AMC

TEST

ME 4543: Mechatronics
Department of Mechanical Engineering
Mock Exam

Useful information:

- (1) There are 4 questions.
- (2) Each question has only 1 correct answer. Each question is worth 1 point and there is no negative marking.
- (3) Cellphones, laptops, tablets and other electronics except calculators should be shut down. Only calculators are allowed.
- (4) Darken the appropriate box next to the options entirely. Your answers will be graded by a computer so it is important that you darken the bubble entirely and do not write anything near the bubbles or options.

NOTE: The actual exam will have 20 questions worth 20 points.

Firstname and Lastname:

Part 1

Question 1 A voltage source $V = 10\text{ V}$, resistors R_1 and $R_2 = 20\ \Omega$ are in all series. If the voltage drop across the R_1 resistor is 2.5 V then R_1 in Ω is


- 5 3.33 6.67 10 7.5

Question 2 Consider two resistances, $R_1 = 5\ \Omega$ and $R_2 = 10\ \Omega$. The two resistors when connected in series, have an effective resistance R_{series} and when connected in parallel, have an effective resistance $R_{parallel}$. Indicate all true statements.

- $R_{parallel} > R_{series}$
- $R_{series} > R_1$
- Two options are true
- Three options are true
- $R_2 > R_{parallel}$

Question 3 Two capacitors of values $2\mu F$ each as connected in series. The equivalent capacitance in μF is

- 8
- 4
- 0.5
- 2
- 1

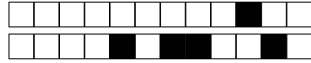


Question 4 A voltage source V_s is connected in series with two resistors $R_1 = 1 \Omega$ and $R_2 = 2 \Omega$. If voltage drop across R_1 is 1 V then V_s in V is

- 1.2
- 0
- 3
- 12
- 8

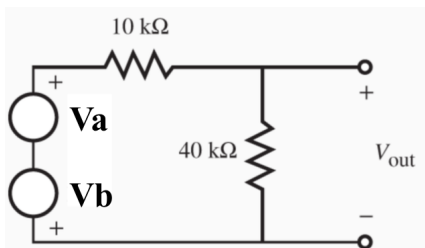Question 5 In the circuit shown if $V_a = 10 \text{ V}$ and $V_b = 5 \text{ V}$ then V_{out} in V equals

- Three options are true
- $R_2 > R_{parallel}$
- $R_{series} > R_1$
- $R_{parallel} > R_{series}$
- Two options are true




Question 6 A resistor has a value of 50 M Ω . The second band is black. The third band will be

- Orange
- Violet
- Blue
- Red

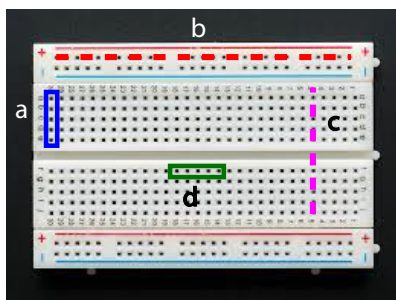Question 7 Consider the breadboard below. Indicate the true statement

- Holes shown by the pink vertical line denoted by c are all connected
- Holes shown by the red dashed line denoted by b are all connected
- Two options are true
- Three options are true
- Holes shown by the blue vertical box denoted by a are all connected





+4/3/49+

Question 8 For the waveform $y(t) = 10 \sin(\pi t) + 5 \cos(\pi t)$, the DC offset is

- 12
- 11
- 0
- 15
- 5



AMC

TEST

ME 4543: Mechatronics
Department of Mechanical Engineering
Mock Exam

Useful information:

- (1) There are 4 questions.
- (2) Each question has only 1 correct answer. Each question is worth 1 point and there is no negative marking.
- (3) Cellphones, laptops, tablets and other electronics except calculators should be shut down. Only calculators are allowed.
- (4) Darken the appropriate box next to the options entirely. Your answers will be graded by a computer so it is important that you darken the bubble entirely and do not write anything near the bubbles or options.

NOTE: The actual exam will have 20 questions worth 20 points.

Firstname and Lastname:

Part 1

Question 1 A resistor has a value of 50 M Ω . The second band is black. The third band will be

- Red
- Orange
- Blue
- Violet

Question 2 Two capacitors of values $2\mu F$ each as connected in series. The equivalent capacitance in μF is


- 4
- 1
- 8
- 0.5
- 2

Question 3 A voltage source $V = 10$ V, resistors R_1 and $R_2 = 20$ Ω are in all series. If the voltage drop across the R_1 resistor is 2.5 V then R_1 in Ω is

- 5 7.5 3.33 6.67 10


Question 4 A voltage source V_s is connected in series with two resistors $R_1 = 1$ Ω and $R_2 = 2$ Ω . If voltage drop across R_1 is 1 V then V_s in V is

- 12
- 0
- 8
- 3
- 1.2

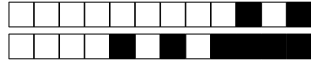

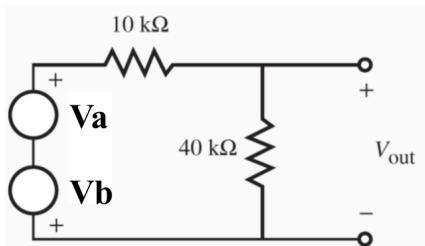
Question 5 In the circuit shown if $V_a = 10\text{ V}$ and $V_b = 5\text{ V}$ then V_{out} in V equals

- Three options are true
- $R_{parallel} > R_{series}$
- $R_{series} > R_1$
- $R_2 > R_{parallel}$
- Two options are true



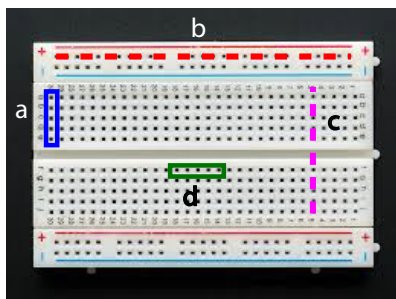Question 6 Consider the breadboard below. Indicate the true statement

- Holes shown by the red dashed line denoted by b are all connected
- Three options are true
- Two options are true
- Holes shown by the blue vertical box denoted by a are all connected
- Holes shown by the pink vertical line denoted by c are all connected



Question 7 For the waveform $y(t) = 10 \sin(\pi t) + 5 \cos(\pi t)$, the DC offset is

- 12
- 5
- 15
- 0
- 11



Question 8 Consider two resistances, $R_1 = 5 \Omega$ and $R_2 = 10 \Omega$. The two resistors when connected in series, have an effective resistance R_{series} and when connected in parallel, have an effective resistance $R_{parallel}$. Indicate all true statements.

- Three options are true
- $R_2 > R_{parallel}$
- Two options are true
- $R_{parallel} > R_{series}$
- $R_{series} > R_1$